

# Electrical Circuits

## Lecture 15: BJT Transistors

By: Mahmoud Momtazpour  
[ceit.aut.ac.ir/~momtazpour](http://ceit.aut.ac.ir/~momtazpour)



# Topic Overview

---


- BJT Large Signal Model
- BJT Modes of Operations
- BJT DC Analysis
- BJT Small Signal Model
- BJT AC Analysis

# BJT

- B: Base
- C: Collector
- E: Emitter

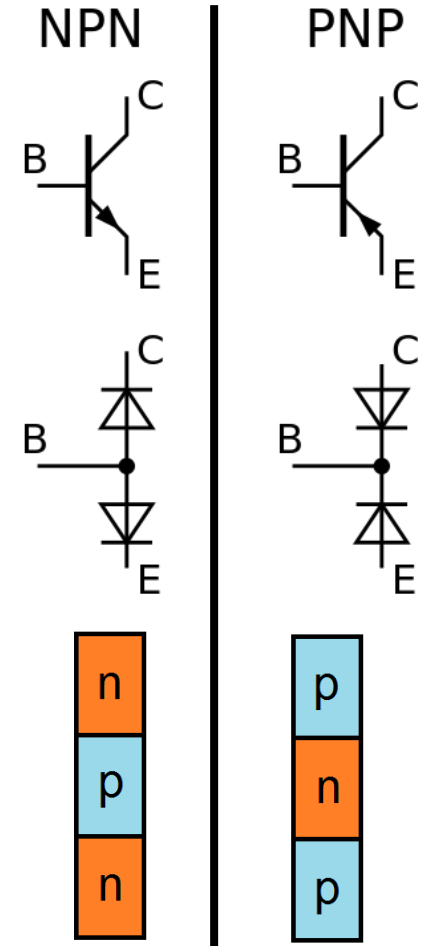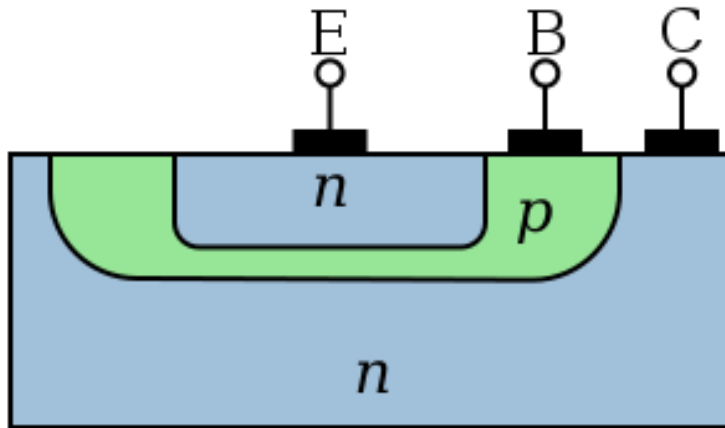


# BJT Operation

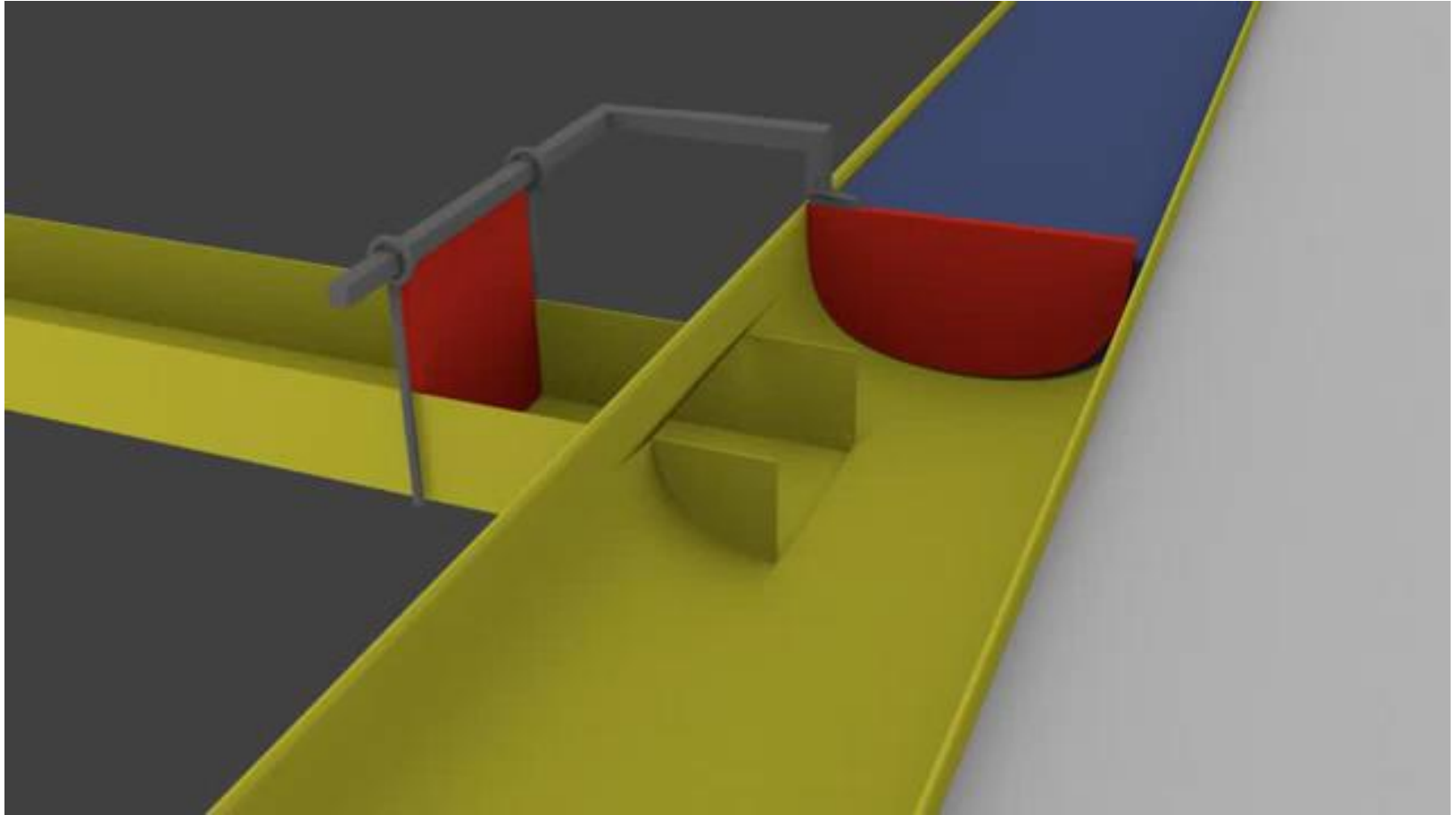
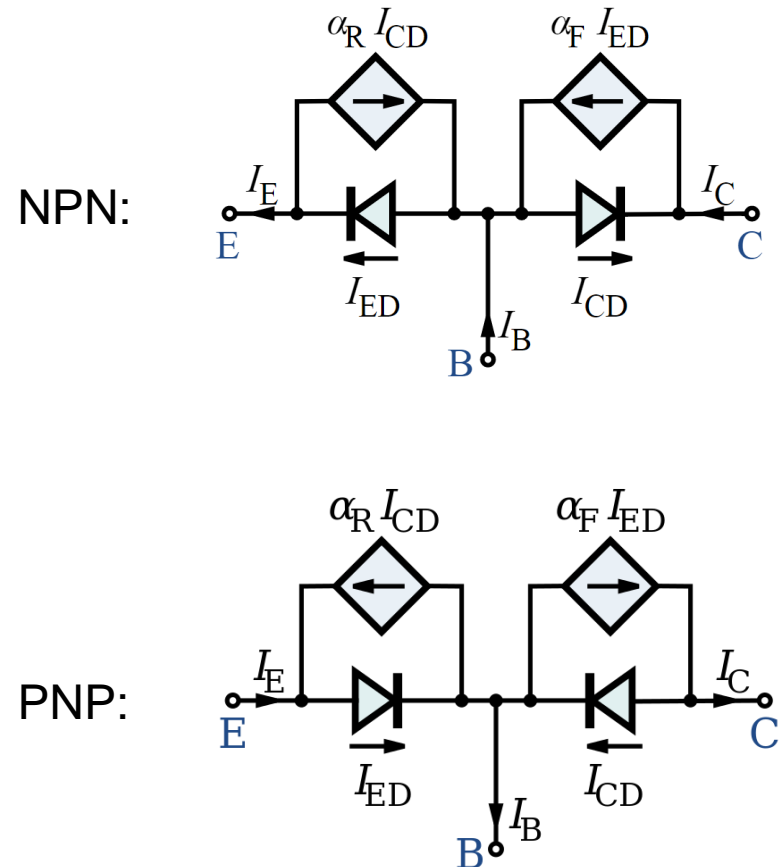
# BJT Large Signal Model

- Ebers-Moll Model
- Modes of operation:
  - ▣ Cut-off
  - ▣ Forward Active
  - ▣ Reverse Active
  - ▣ Saturation




# NPN BJT Modes of Operation

## □ Cut-off

- $V_B - V_C < 0.4$

- $V_B - V_E < 0.6$


- $I_B = I_C = I_E = 0$

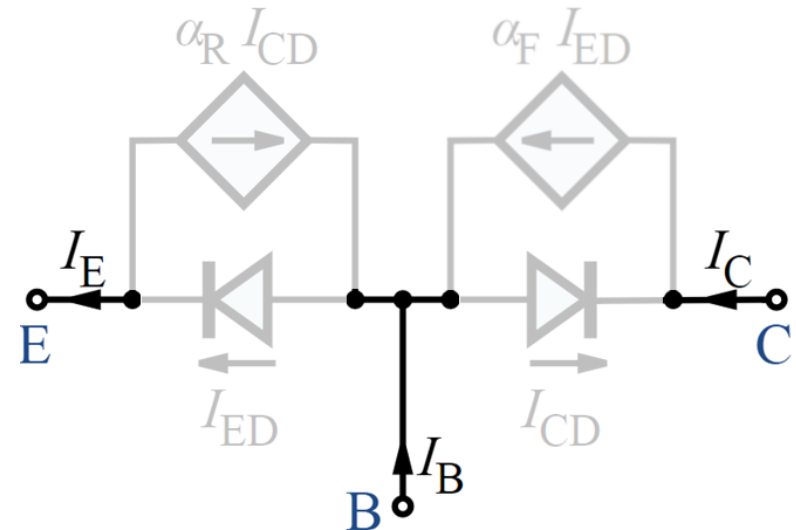

# NPN BJT Modes of Operation

## □ Forward Active

- $V_B - V_C < 0.4$
- $V_B - V_E > 0.6$

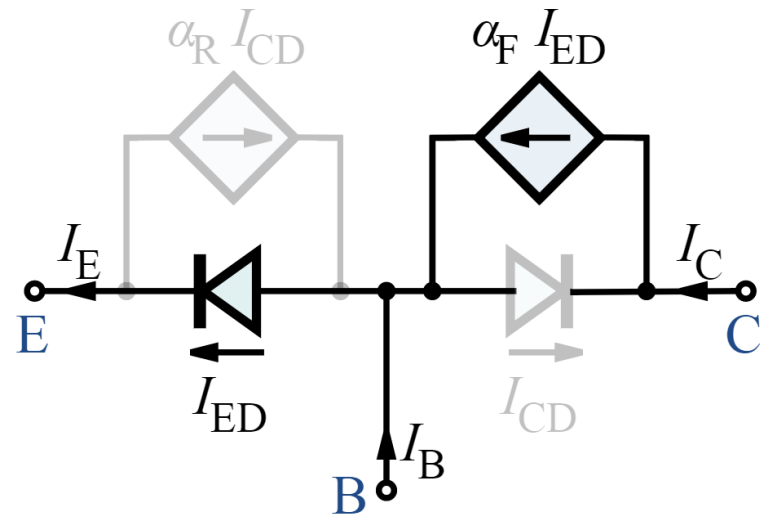


## □ Acts as an amplifier!

- $I_C = \alpha I_E \quad (0.98 < \alpha < 0.998)$
- $I_E = I_B + I_C$
- $I_C = \beta I_B$
- $\beta = \frac{\alpha}{1-\alpha}$

# NPN BJT Modes of Operation

## □ Reverse Active

- $V_B - V_C > 0.4$
- $V_B - V_E < 0.6$

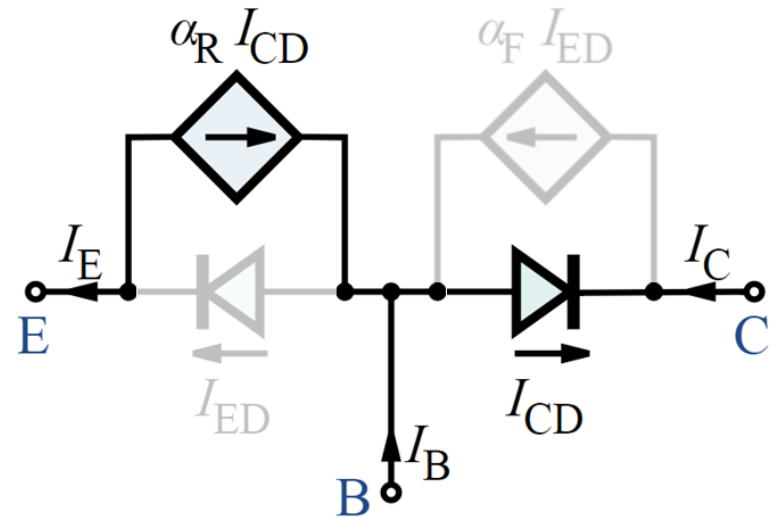


- The collector diode is built in a way that it can tolerate large reverse biases, but emitter diode can't.
- It also has poor  $\beta$ .
- So, we usually don't use BJTs in this mode...



# NPN BJT Modes of Operation

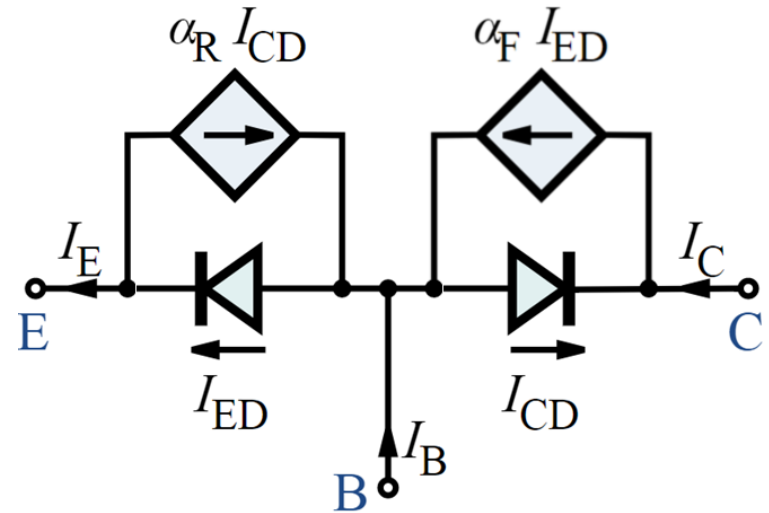
## □ Saturation

- $V_B - V_C > 0.4$
- $V_B - V_E > 0.6$
- $V_C - V_E \approx 0.2$




- Acts as a switch!
- 0.2 is called  $V_{sat}$
- $I_C < \beta I_B$  ( $I_C$  is set by the circuit, not by  $I_B$ )


# BJT Configurations

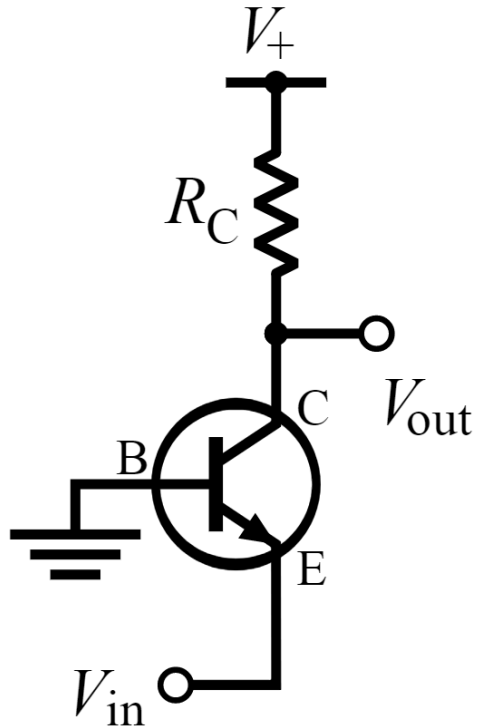

Common Base

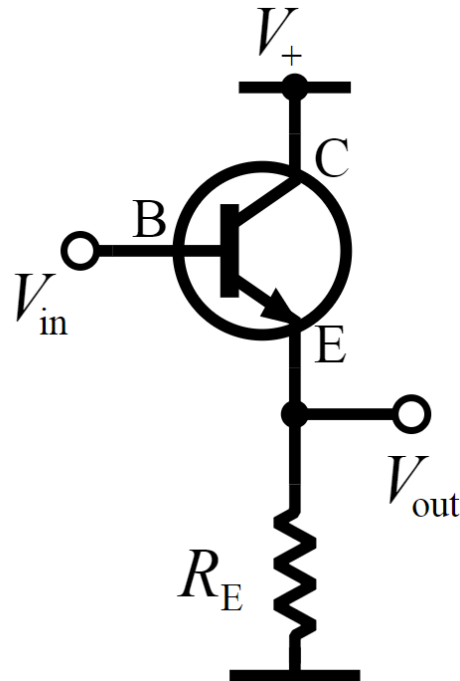

Common Collector

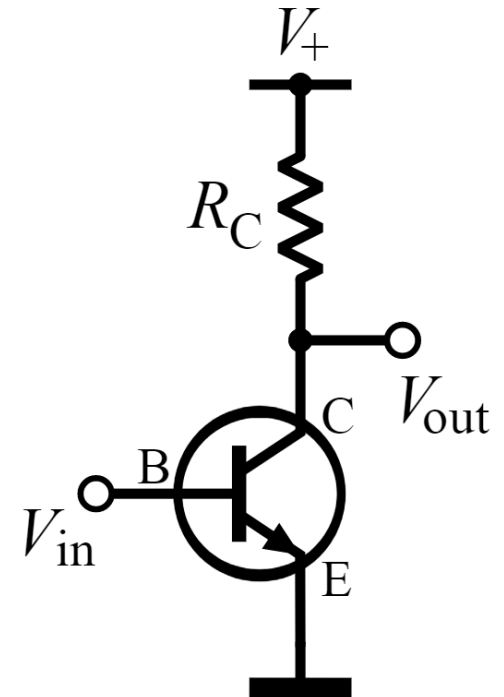

Common Emitter

# BJT DC Analysis

- Write BE and CE KVLs
- Assume Cut-off ( $I_B = 0$ ), use BE-KVL to find  $V_{BE}$ :
  - ▣ If  $V_{BE} < 0.6$ , OK!  $I_C = 0$ , Use CE-KVL to find  $V_{CE}$ .
  - ▣ If  $V_{BE} > 0.6$ , assumption is not true...
- Assume Active ( $V_{BE} > 0.6$ ), assume  $V_{BE} = 0.6$ , use BE-KVL to find  $I_B$ . Find  $I_C = \beta I_B$ . Use CE-KVL to find  $V_{CE}$ .
  - ▣ If  $V_{CE} > 0.2$ , OK! Otherwise, assumption is not true
- Assume Saturation ( $V_{CE} = 0.2$ ). Use CE-KVL to find  $I_C$ . Double Check  $I_C < \beta I_B$

# Example

- Find  $i_C$  ( $\beta = 100$ )
- Write BE and CE KVLs:
  - ▣  $-4 + 40000i_B + v_{BE} = 0$
  - ▣  $-12 + 1000i_C + v_{CE} = 0$
- Assume Cut-off
  - ▣  $i_B = 0 \rightarrow v_{BE} = 4 > 0.6$
- Assume Active
  - ▣  $v_{BE} = 0.6 \rightarrow i_B = \frac{4-0.6}{40000} = 85\mu A > 0$
  - ▣  $i_C = 100 \times 85\mu = 8.5mA \rightarrow v_{CE} = 3.5 > 0.2$

